

UNIT-3: BOOLEAN ALGEBRA AND LOGIC GATES(4 Hrs)

Topics covered:

- Basic definition, Basic properties and theorem of Boolean algebra, DeMorgan's theorem,
- Logic gates and truth tables, Universality of NAND and NOR gates, Trio-stage logic.

- ✓ Logic gates are the fundamental building blocks of digital systems.
- ✓ The name logic gate is derived from the ability of such devices to make decisions, in the sense that it produces one output level when some combinations of input levels are present

➤ Inputs & Outputs for Logic Circuits

- ✓ Input & Output of logic gates can occur only in two levels.

HIGH

LOW

True

False

ON

OFF


1

0

➤ Truth Table

- ✓ A table which lists all the possible combinations of input variables and the corresponding outputs is called a “Truth Table”.
- ✓ It shows how the logic circuits output responds to various combinations of logic levels at the inputs

Switches in parallel => OR

 


Switch 1	Switch 2	Output
OFF	OFF	OFF
OFF	ON	GLOW
ON	OFF	GLOW
ON	ON	GLOW

➤ Logic


- ✓ A logic in which the voltage levels represent logic 1 and logic 0.
- ✓ Level logic may be Positive or Negative.
- ✓ A **“Positive Logic”** is the one which the higher of the two voltage levels represents the logic 1 and the lower of the two voltage level represents the logic 0.
- ✓ A **“Negative Logic”** is the one which the lower of the two voltage levels represents the logic 1 and the higher of the two voltage level represents the logic 0.

Logic Gates

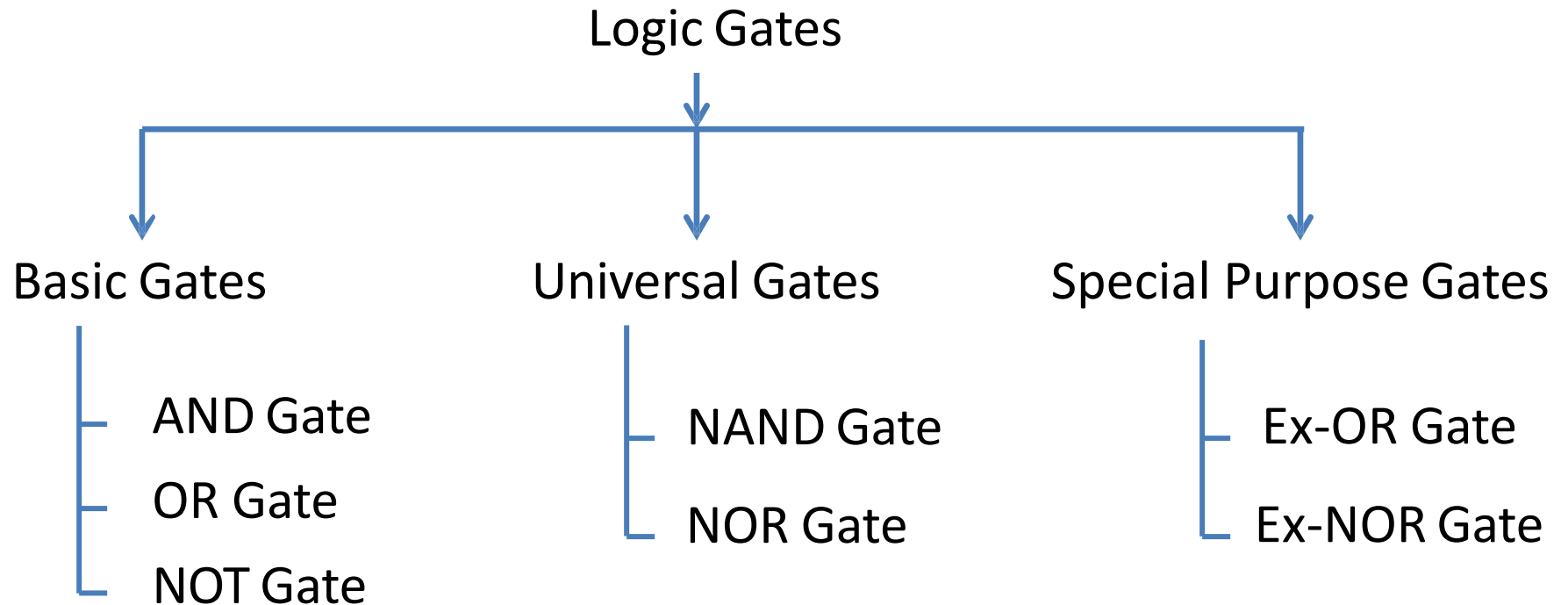


AND Gate

 - ✓ An AND gate has two or more inputs but only one output.
- ✓ The output assumes the logic 1 state, when both inputs are at logic 1 state.
- ✓ The output assumes the logic 0 state even if one of its inputs is at logic 0 state.




AND Gate

 


Inputs		Output
A	B	$Y = A.B$
0	0	0

AND Gate

 


Inputs		Output
A	B	$Y = A.B$
0	0	0
0	1	0

AND Gate

 

Inputs		Output
A	B	$Y = A.B$
0	0	0
0	1	0
1	0	0


AND Gate

 


Inputs		Output
A	B	$Y = A.B$
0	0	0
0	1	0
1	0	0
1	1	1

3 - Input AND Gate

 3 – Input AND Gate using 2 – Input AND Gate



Symbol : 3 – Input AND Gate

 


Truth Table : 3 – Input AND Gate

Input			Output $Y = A.B.C$
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

OR Gate

 
- ✓ An OR gate has two or more inputs but only one output.
- ✓ The output assumes the logic 1 state, when even if one of its inputs is in logic 1 state.
- ✓ The output assumes the logic 0 state only when both the inputs are in logic 0 state.



Prakash khanal, NCIT


Logic Symbol

OR Gate

 


Inputs		Output
A	B	$Y = A + B$
0	0	0

OR Gate

 


Inputs		Output
A	B	$Y = A + B$
0	0	0
0	1	1

OR Gate

 

Inputs		Output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1


OR Gate

 


Inputs		Output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Three Input OR Gate

 3 – Input OR Gate using 2 – Input OR Gate



Symbol : 3 – Input OR Gate

 


Truth Table : 3 – Input OR Gate


Input			Output $Y = A + B + C$
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

NOT Gate (Inverter)

 - ✓ A NOT gate, also called inverter, has only one input and of course only one output.
- ✓ It is a device whose output is always the complement of its input.
- ✓ That is, the output of a NOT gate assumes the logic 1 state when its input is in logic 0 state and vice versa.




NOT Gate

 

Input	Output
A	$Y = \bar{A}$
0	1

NOT Gate

 


Input	Output
A	$Y = \bar{A}$
0	1
1	0

Universal Gates (NAND and NOR Gate)

- ✓ NAND and NOR gates are Universal Gates.
- ✓ Both NAND and NOR gates can perform all the three basic logic functions (AND, OR and NOT).
- ✓ Therefore, AOI logic can be converted to NAND logic or NOR logic


NAND Gate

 - ✓ NAND means NOT AND i.e. AND output is inverted.
- ✓ So NAND gate is a combination of an AND gate and a NOT gate.




NAND Gate

 - ✓ The output is logic 0 level, only when all the inputs are logic 1 level.
- ✓ For any other combination of inputs, the output is a logic 1 level.




Logic Symbol

NAND Gate

 


Inputs		Output
A	B	$Y = \overline{A.B}$
0	0	1

NAND Gate

 


Inputs		Output
A	B	$Y = \overline{A.B}$
0	0	1
0	1	1

NAND Gate

 

Inputs		Output
A	B	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1


NAND Gate

 

Inputs		Output
A	B	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0


NOR Gate

 - ✓ NOR means NOT OR i.e. OR output is inverted.
- ✓ So NOR gate is a combination of an OR gate and a NOT gate.




NOR Gate

 - ✓ The output is logic 1 level, only when all the inputs are logic 0 level.
- ✓ For any other combination of inputs, the output is a logic 0 level.




Logic Symbol

NOR Gate

 


Inputs		Output
A	B	$Y = \overline{A+B}$
0	0	1

NOR Gate

 


Inputs		Output
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0

NOR Gate

 

Inputs		Output
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0



NOR Gate

 

Inputs		Output
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0



Universal Gate

NOT Gate using NAND Gate

  



Universal Gate

AND Gate using NAND Gate

  

Universal Gate

OR Gate using NAND Gate

 
 


$Y = \overline{\overline{A} \cdot \overline{B}}$
 $Y = \overline{\overline{A}} + \overline{\overline{B}}$ (Demorgan's Theorem)

$$Y = A + B$$



Universal Gate

NOR Gate using NAND Gate

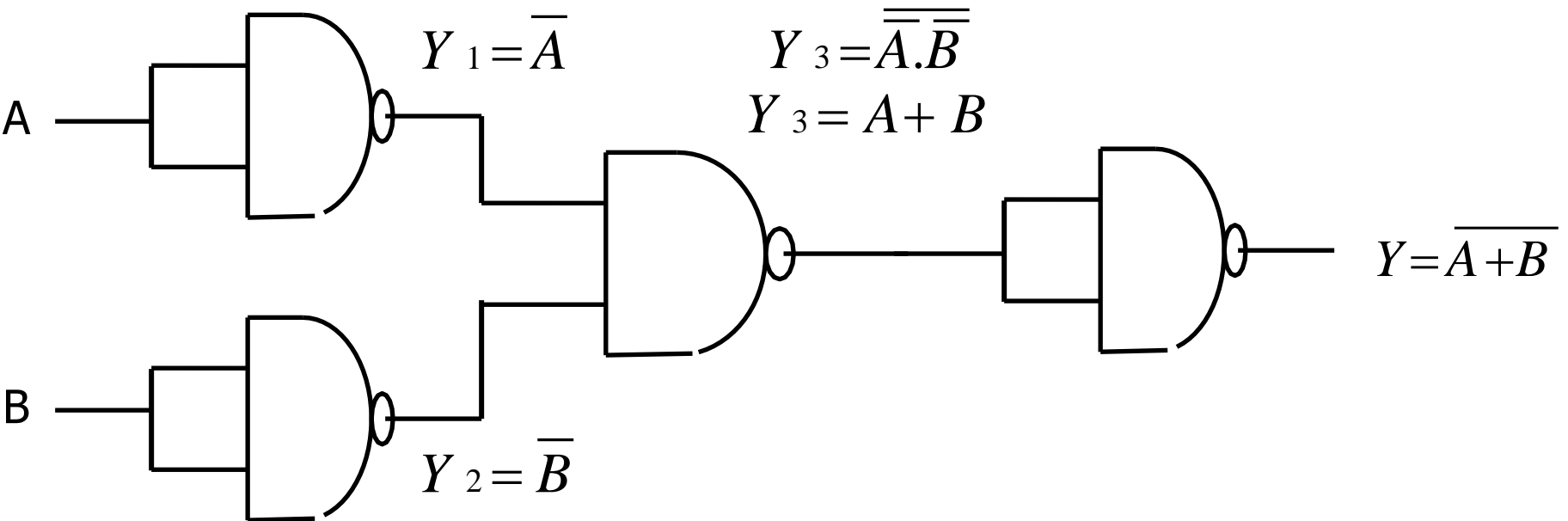 



Universal Gate

NOT Gate using NOR Gate

  



Universal Gate

OR Gate using NOR Gate

  

Universal Gate

AND Gate using NOR Gate

  

$$Y = \overline{\overline{A} + \overline{B}}$$



$$Y = \overline{\overline{A}} \cdot \overline{\overline{B}}$$

$$Y = A.B$$

(Demorgan's Theorem)

Universal Gate

NAND Gate using NOR Gate

  


Special Purpose Gate – Ex-OR Gate

- ✓ An Ex-OR gate is two input, one output logic circuit.
- ✓ The output assumes the logic 1 state, when one and only one of its two inputs assumes a logic 1 state.
- ✓ Under the conditions when both the inputs assume the logic 0 state or logic 1 state, the output assumes logic 0.

Ex-OR Gate

 - ✓ If input variables are represented by A and B and the output variable by Y the representation for the output of this gate is as




$$Y = A \oplus B$$

$$Y = \bar{A}B + A\bar{B}$$

Logic Symbol


Logic Expression

Ex-OR Gate

 


Inputs		Output
A	B	$Y = A \oplus B$
0	0	0

Ex-OR Gate

 


Inputs		Output
A	B	$Y = A \oplus B$
0	0	0
0	1	1

Ex-OR Gate

 



Inputs		Output
A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1

Ex-OR Gate

 

Inputs		Output
A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

3 – Input Ex-OR Gate

  


INPUT			OUTPUT
A	B	C	$Y = A \oplus B \oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Special Purpose Gate – Ex-NOR Gate

- ✓ An Ex-NOR gate is two input, one output logic circuit.
- ✓ The output assumes a logic 0 state, when one of the input assumes a logic 0 state and other a logic 1 state.
- ✓ The output assumes a logic 1 state only when both the inputs assume a logic 0 state or when both the inputs assume a logic state.

Ex-NOR Gate

 - ✓ If input variables are represented by A and B and the output variable by Y the representation for the output of this gate is as




$$Y = A \odot B$$

$$Y = AB + \bar{A}\bar{B}$$

Logic Symbol


Logic Expression

Ex-NOR Gate

 


Inputs		Output
A	B	$Y = A \odot B$
0	0	1

Ex-NOR Gate

 


Inputs		Output
A	B	$Y = A \odot B$
0	0	1
0	1	0

Ex-NOR Gate

 



Inputs		Output
A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0

Ex-NOR Gate

 

Inputs		Output
A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

3 – Input Ex-NOR Gate

  

INPUT			OUTPUT
A	B	C	$Y = A \odot B \odot C$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- ✓ Boolean Algebra is used to analyze and simplify the digital (Logic) circuit.
- ✓ Since it uses only the binary numbers i.e. 0 and 1 it is also called as “Binary Algebra” or “Logical Algebra”.

Boolean Algebra

- ✓ The rules of Boolean Algebra are different from those of the conventional algebra.
- ✓ It is invented by George Boole in the year 1854.

➤ Axioms

- ✓ Axioms or postulates of Boolean algebra are set of logical expressions that we accept without proof and upon which we can build a set of useful theorems.
- ✓ Actually, axioms are nothing more than the definitions of the three basic logic operations that we have already discussed AND, OR and INVERT.

➤ Axioms

AND Operation

Axiom 1: $0 . 0 = 0$

Axiom 2: $0 . 1 = 0$

Axiom 3: $1 . 0 = 0$

Axiom 4: $1 . 1 = 1$

➤ Axioms

OR Operation

Axiom 5: $0 + 0 = 0$

Axiom 6: $0 + 1 = 1$

Axiom 7: $1 + 0 = 1$

Axiom 8: $1 + 1 = 1$

➤ Axioms

NOT Operation

Axiom 9: $\bar{1} = 0$

Axiom 10: $\bar{0} = 1$

➤ Inversion Law (or Complementation Law)

✓ The term complement means to invert i.e. to change 0's to 1's and 1's to 0's.

Law 1: $\bar{1} = 0$

Law 2: $\bar{0} = 1$

Law 3: If $A=0$, then $A = \bar{1}$

Law 4: If $A=1$, then $A = \bar{0}$

Law 5: $\bar{\bar{A}} = A$ (Double Inversion Law)

➤ AND Laws

Law 1: $A \cdot 0 = 0$ Null Law

Law 2: $A \cdot 1 = A$ Identity Law

Law 3: $A \cdot A = A$

Law 4: $A \cdot \bar{A} = 0$

➤ OR Laws

Law 1: $A + 0 = A$ Null Law

Law 2: $A + 1 = 1$ Identity Law

Law 3: $A + A = A$

Law 4: $A + \overline{A} = 1$

➤ Commutative Laws


$$\text{Law 1: } A+B = B+A$$

- ✓ This Law states that, A OR B is the same as B OR A
i.e. the order in which the variables are ORed is immaterial.
- ✓ This means that it makes no difference which input of an OR gate is connected to A and which to B.


Boolean Algebra

Proof:


$A+B$

 

Inputs		Output
A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

 

$B+A$

 

Inputs		Output
B	A	$Y=B+A$
0	0	0
0	1	1
1	0	1
1	1	1

➤ Commutative Laws

- ✓ This law can be extended to any number of variables. For example,

$$A+B+C = B+C+A = C+A+B = B+A+C$$

➤ Commutative Laws


$$\text{Law 2: } A.B = B.A$$

- ✓ This Law states that, A AND B is the same as B AND A i.e. the order in which the variables are ANDed is immaterial.
- ✓ This means that it makes no difference which input of an AND gate is connected to A and which to B.


Boolean Algebra

Proof:


$A.B$

 

$B.A$

 

Inputs		Output
A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1

 

Inputs		Output
B	A	$Y=B.A$
0	0	0
0	1	0
1	0	0
1	1	1

➤ Commutative Laws

✓ This law can be extended to any number of variables. For example,

$$A.B.C = B.C.A = C.A.B = B.A.C$$

➤ Associative Laws



Law 1: $(A+B)+C = A+(B+C)$

- ✓ A OR B ORed with C is the same as A ORed with B OR C.
- ✓ This law states that the way the variables are grouped and ORed is immaterial.


Boolean Algebra

Proof:

$$(A+B)+C$$

  

$$A+(B+C)$$

 

A	B	C	A+B	$(A+B)+C$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A	B	C	B+C	$A+(B+C)$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

➤ Associative Laws

- ✓ This law can be extended to any number of variables. For example,

$$A+(B+C+D) = (A+B+C)+D = (A+B)+(C+D)$$

➤ Associative Laws



$$\text{Law 2: } (A.B).C = A.(B.C)$$

- ✓ A AND B ANDed with C is the same as A ANDed with B AND C.
- ✓ This law states that the way the variables are grouped and ANDed is immaterial.


Boolean Algebra

Proof:

$(A.B).C$

  

$A.(B.C)$

 

A	B	C	A.B	$(A.B).C$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1

A	B	C	B.C	$A.(B.C)$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

➤ Associative Laws

- ✓ This law can be extended to any number of variables. For example,

$$A.(B.C.D) = (A.B.C).D = (A.B).(C.D)$$

➤ Distributive Laws


$$\text{Law 1: } A(B+C) = AB+AC$$

- ✓ This law states that ORing of several variables and ANDing the result with a single variable is equivalent to ANDing that single variable with each of the several variables and then ORing the products.

Boolean Algebra


Proof:

$$A.(B+C)$$

 

A	B	C	B+C	A(B+C)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

$$AB+AC$$

 

A	B	C	AB	AC	AB+AC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

➤ Distributive Laws

- ✓ This law can be extended to any number of variables. For example,

$$ABC(D+E) = ABCD + ABCE$$

$$AB(CD+EF) = ABCD + ABEF$$

➤ Distributive Laws



$$\text{Law 2: } A+BC = (A+B).(A+C)$$

- ✓ This law states that ANDing of several variables and ORing the result with a single variable is equivalent to ORing that single variable with each of the several variables and then ANDing the products.


Boolean Algebra

Proof:

$$A + (B.C)$$

  

$$(A+B).(A+C)$$

 

A	B	C	BC	A+BC
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	B	C	A+B	A+C	(A+B). (A+C)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

➤ Redundant Literal Rule


$$\text{Law 1: } A + \bar{A}B = A + B$$

- ✓ This law states that ORing of variable with the AND of the complement of that variable with another variable, is equal to the ORing of the two variables


Boolean Algebra

Proof:


$$A + \bar{A}B$$

 

$$A + B$$

 

A	B	$\bar{A}B$	$A + \bar{A}B$
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	1

 

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

➤ Redundant Literal Rule


$$\text{Law 2: } A(\bar{A} + B) = A.B$$

- ✓ This law states that ANDing of variable with the OR of the complement of that variable with another variable, is equal to the ANDing of the two variables


Boolean Algebra

Proof:


$$A(\bar{A} + B)$$

 

$$A.B$$

 


A	B	$\bar{A} + B$	$A(\bar{A} + B)$
0	0	1	0
0	1	1	0
1	0	0	0
1	1	1	1

 

A	B	$A.B$
0	0	0
0	1	0
1	0	0
1	1	1

➤ Idempotence Laws


Law 1: $A.A = A$

 

- ✓ Idempotence means the same value
- ✓ If $A=0$, then $A.A = 0.0 = 0 = A$
- ✓ If $A=1$, then $A.A = 1.1 = 1 = A$
- ✓ This law states that ANDing of a variable with itself is equal to that variable only.

➤ Idempotence Laws

Law 2: $A + A = A$

 

- ✓ Idempotence means the same value
- ✓ If $A=0$, then $A+A = 0+0 = 0 = A$
- ✓ If $A=1$, then $A+A = 1+1 = 1 = A$
- ✓ This law states that ORing of a variable with itself is equal to that variable only.

➤ Absorption Laws

$$\text{Law 1: } A + A.B = A$$

✓ This law states that ORing of a variable with AND of that variable and another variable is equal to that variable itself.

✓ Therefore,


$$A + A. \text{ Any Term} = A$$

Boolean Algebra

Proof:

$$A + A.B$$

$$A$$

 

A	B	$A.B$	$A + A.B$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

➤ Absorption Laws

$$\text{Law 2: } A(A + B) = A$$

✓ This law states that ANDing of a variable with OR of that variable and another variable is equal to that variable itself.


✓ Therefore,

$$A \cdot (A + \text{Any Term}) = A$$

Boolean Algebra

Proof:

$$A(A + B) = A$$

 

A	B	$A + B$	$A(A + B)$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

➤ De-Morgan's Theorem




First Theorem: $\overline{A + B} = \bar{A} . \bar{B}$

- ✓ This theorem states that the complement of a sum of variables is equal to the product of their individual complements.
- ✓ What it means is that the complement of two or more variables ORed together, is the same as the AND of the complements of each of the individual variables

Boolean Algebra




Proof: Logic Diagram

L.H.S.

   

NOR Gate

R.H.S.

   


Bubbled AND Gate

Boolean Algebra

Proof: Logic Table

$$\overline{A+B}$$

A	B	$A+B$	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 

$$\bar{A}.\bar{B}$$

A	B	\bar{A}	\bar{B}	$\bar{A}.\bar{B}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

➤ De-Morgan's Theorem

✓ This law can be extended to any number of variables. For example,

$$\overline{A+B+C+D+\dots\dots\dots} = \overline{A}.\overline{B}.\overline{C}.\overline{D}\dots\dots\dots$$

$$\overline{AB+CD+EFG+\dots\dots\dots} = (\overline{AB}).(\overline{CD}).(\overline{EFG})\dots\dots\dots$$

➤ De-Morgan's Theorem




Second Theorem: $\overline{A.B} = \bar{A} + \bar{B}$

- ✓ This theorem states that the complement of a product of variables is equal to the sum of their individual complements.
- ✓ What it means is that the complement of two or more variables ANDed together, is the same as the OR of the complements of each of the individual variables

Boolean Algebra




Proof: Logic Diagram

L.H.S.

   

NAND Gate

R.H.S.

   


Bubbled OR Gate

Boolean Algebra

Proof:

$$\overline{A.B}$$

 

$$\bar{A} + \bar{B}$$

A	B	$A.B$	$\overline{A.B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

➤ De-Morgan's Theorem

- ✓ This law can be extended to any number of variables. For example,

$$\overline{A.B.C.D.....} = \bar{A} + \bar{B} + \bar{C} + \bar{D} +$$

$$\overline{(AB)(CD)(EFG).....} = \overline{AB} + \overline{CD} + \overline{EFG} +$$

- ✓ Duality represents relation between expressions in positive logic system and expression in negative logic system.

- ✓ The distinction between positive and negative logic system is important.
- ✓ An OR gate in positive logic system becomes an AND gate in negative logic system and vice versa.
- ✓ Positive & negative logics thus give rise to a basic duality in all Boolean identities.

- ✓ When changing from one logic system to another 0 becomes 1 and 1 becomes 0.
- ✓ Furthermore, an AND gate becomes an OR gate and an OR gate becomes AND gate.

Duality

- ✓ Given Boolean identity, we can produce a dual identity by changing all '+' signs to ' signs, all ' signs to '+' signs and complementing all 0's and 1's.
- ✓ The variables are not complemented in this process.

Examples of Dual Identities


Sr. No.	Given Expression	Dual
1	$\bar{0} = 1$	$\bar{1} = 0$
2	$0.1 = 0$	$1 + 0 = 1$
3	$0.0 = 0$	$1 + 1 = 1$
4	$1.1 = 1$	$0 + 0 = 0$
5	$A.0 = 0$	$A + 1 = 1$
6	$A.1 = A$	$A + 0 = A$

Examples of Dual Identities

Sr. No.	Given Expression	Dual
7	$A.B = B.A$	$A + B = B + A$
8	$A.(B.C) = (A.B).C$	$A + (B + C) = (A + B) + C$
9	$A.(B + C) = A.B + A.C$	$A + BC = (A + B)(A + C)$
10	$A.(A + B) = A$	$A + AB = A$
11	$A.(A.B) = A.B$	$A + A + B = A + B$
12	$\overline{A.B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}.\bar{B}$
13	$(A + B)(\bar{A} + \bar{C}) = (A + B)(\bar{A} + \bar{C})$	$AB + \bar{A}\bar{C} = AB + \bar{A}\bar{C}$

TRI-STATE LOGIC

- In digital electronics **three-state**, **tri-state**, or **3-state** logic allows an output port to assume a high impedance state, effectively removing the output from the circuit, in addition to the 0 and 1 logic levels.
- Three-state outputs are implemented in many registers, bus drivers and flip-flops in the 7400 and 4000 series as well as in other types, but also internally in many integrated circuits.

 

A tristate buffer can be thought of as a switch. If *B* is on, the switch is closed. If *B* is off, the switch is open

Example 1

Reduce the following Boolean Expression using Boolean Laws:

$$A.\overline{B} + \overline{A}.B + A.B + \overline{A}.\overline{B}$$

Example 1

Reduce the following Boolean Expression using Boolean Laws:

$$A.\bar{B} + \bar{A}.B + A.B + \bar{A}.\bar{B}$$

$$= A.\bar{B} + \bar{A}.B + A.B + \bar{A}.B$$

$$= A.\bar{B} + A.B + \bar{A}.B + \bar{A}.B$$

$$= A.(\bar{B} + B) + \bar{A}(B + B) \quad (B + B = 1)$$

$$= A + A \quad (A + \bar{A} = 1)$$

$$= 1$$

$$A.\bar{B} + \bar{A}.B + A.B + \bar{A}.\bar{B} = 1$$

Example 2

Reduce the following Boolean Expression using Boolean Laws:

$$\overline{A}\overline{B}C + \overline{A}BC + ABC$$

Example 2

Reduce the following Boolean Expression using Boolean Laws:

$$\overline{A}\overline{B}C + \overline{A}BC + ABC$$

$$= \overline{A}\overline{B}C + \overline{A}BC + ABC$$

$$= \overline{A}\overline{B}C + BC(\overline{A} + A)$$

$$= \overline{A}\overline{B}C + BC \quad (A + \overline{A} = 1)$$

$$= C(\overline{A}\overline{B} + B)$$

$$= C(B + A)(\overline{B} + B) \quad (\text{Distributive Law})$$

$$= C(B + A) \quad (\overline{B} + B = 1)$$

$$= AC + BC$$


Example 3

Realize $Y=AB+AC$ using one OR gate and one AND gate

Example 3

Realize $Y=AB+AC$ using one OR gate and one AND gate

$$Y = AB + AC$$

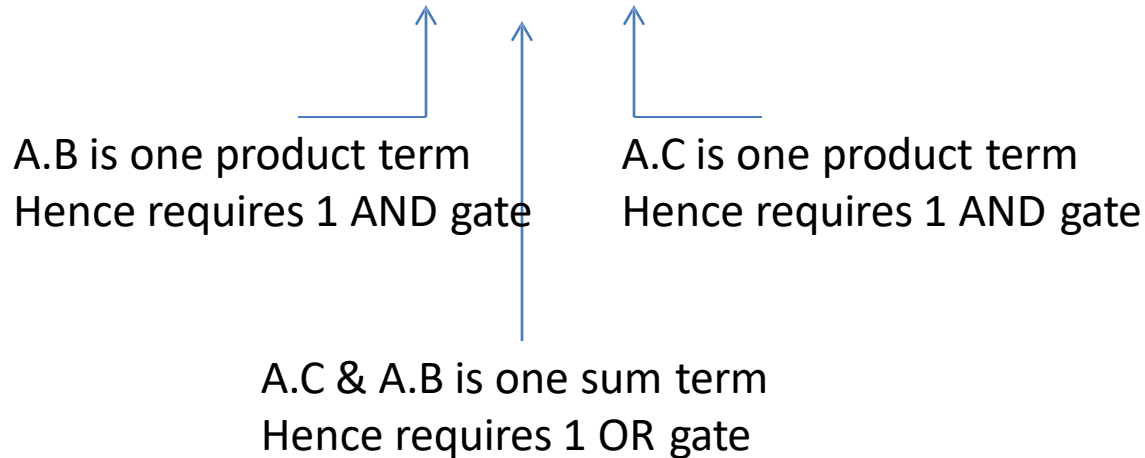


Hence to implement $Y=AB+AC$ equation we require 2 AND gates and 1 OR gate

But we have to use only 1 AND gate and 1 OR gate

Hence simplification is necessary

$$Y = AB + AC$$

$$Y = A(B + C)$$

 

Example 4

Prove that:

$$A + \bar{A}B = A + B$$

Example 4

Prove that:

$$A + \bar{A}B = A + B$$

$$\begin{aligned}\text{L.H.S} &= A + \bar{A}B \\ &= A(1) + \bar{A}B \\ &= A(1 + B) + \bar{A}B \\ &= A + AB + \bar{A}B \\ &= A + B(A + \bar{A}) \\ &= A + B \quad (A + \bar{A} = 1)\end{aligned}$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 5

Prove that:

$$(A + B)(A + \overline{B}) = A$$

Example 5

Prove that:

$$(A + B)(A + \bar{B}) = A$$

$$\text{L.H.S} = (A + B)(A + \bar{B})$$

$$= AA + A\bar{B} + AB + B\bar{B}$$

$$= A + A\bar{B} + AB + 0 \quad (AA=A, B\bar{B}=0)$$

$$= A + A(\bar{B} + B)$$

$$= A + A \quad (\bar{B} + B = 1)$$

$$= A \quad (A + A = A)$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 6

With the help of Boolean Laws, Prove that:

$$(A + \bar{B} + AB)(A + B).\bar{A}\bar{B} = 0$$

Example 6

With the help of Boolean Laws, Prove that:

$$(A + \bar{B} + AB)(A + B).\bar{A}\bar{B} = 0$$

$$\begin{aligned}\text{L.H.S.} &= (A + \bar{B} + AB)(A + B).\bar{A}\bar{B} \\ &= (A + \bar{B} + AB)(A\bar{A}\bar{B} + AB\bar{B})\end{aligned}$$

$$= (A + \bar{B} + AB).(0) \quad \left(A.\bar{A}=0, B.\bar{B}=0 \right)$$

$$= 0$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 7

With the help of Boolean Laws, Prove that:

$$AB + \bar{A}B + \bar{A}\bar{B} = \bar{A} + B$$

Example 7

With the help of Boolean Laws, Prove that:

$$AB + \bar{A}B + \bar{A}\bar{B} = \bar{A} + B$$

$$\text{L.H.S.} = AB + \bar{A}B + \bar{A}\bar{B}$$

$$= \bar{A}B + \bar{A}\bar{B} + AB$$

$$= \bar{A}(B + \bar{B}) + AB$$

$$= \bar{A} + AB \quad (B + \bar{B} = 1)$$

$$= (A + \bar{A})(\bar{A} + B) \quad (\bar{A} + AB = (\bar{A} + A)(\bar{A} + B))$$

$$= 1.(\bar{A} + B) \quad (A + \bar{A} = 1)$$

$$= \bar{A} + B$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 8

Simplify; $F = XY + XYZ + XYZ + X\bar{Z}Y$

Example 8

Simplify; $F = XY + XYZ + XYZ + X\bar{Z}Y$

$$F = XY + XYZ + XYZ + X\bar{Z}Y$$

$$= XY + XYZ + X\bar{Z}Y \quad (XYZ + XYZ = XYZ)$$

$$= XY(1 + Z + \bar{Z})$$

$$= XY \quad (1 + Z + \bar{Z} = 1)$$

$$= XY$$

Example 9

Prove that;

$$AB + ABC + A\bar{B} = A$$

Example 9

Prove that; $AB + ABC + A\bar{B} = A$

$$\begin{aligned} L.H.S. &= AB + ABC + A\bar{B} \\ &= AB(1 + C) + A\bar{B} \\ &= AB + A\bar{B} & (1 + C = 1) \\ &= A(B + \bar{B}) \\ &= A & (B + \bar{B} = 1) \end{aligned}$$

$$L.H.S = R.H.S$$

IC Chip Manufacturing Process

- ✓ Small Scale Integration (SSI)
- ✓ Medium Scale Integration (MSI)
- ✓ Large Scale Integration (LSI)
- ✓ Very Large Scale Integration (VLSI)
- ✓ Ultra Large Scale Integration (ULSI)
- ✓ Giant Scale Integration (GSI)

- Gate/transistor ratio is roughly
 - SSI < 12 gates/chip
 - MSI < 100 gates/chip
 - LSI ...1K gates/chip
 - VLSI ...10K gates/chip
 - ULSI ...100K gates/chip
 - GSI ...1Meg gates/chip

- ✓ A prediction made by Moore (a co-founder of Intel) in 1965: "... a number of transistors to double every 2 years."