

Question for MOCK Test:

1. What are universal gates? why they are called so? Realize basic gates using universal gates. Also construct NAND gates using NOR gates and NOR gates using NAND gates. 10
2. Design a combinational circuit using PLD device as PLA(4*8*4) that is used to implement full adder function in which sum is represented as s_i and carry as c_i . 10
3. Implement the following function with appropriate MUX. 10
 - I. $F(A,B,C) = \sum(1,4,5,6)$
 - II. $F(A,B,C,D) = \sum(0,1,3,8,9,15)$
4. Design a combinational circuit that convert binary number to excess 3 code to 8,4,-2,-1 code. 10
5. Define counter. Design a BCD counter that counts the binary number from 0000 to 1001 and returns to 0000 to repeat the sequence using T flipflop. 10
6. Draw arithmetic circuit Logic diagram with function table that perform 8 different major function, What is shift register? Draw the block diagram for shifting the content of register A to register B. Describe the operation.