 


Q.N.1.


Ans. NAND and NOR gates are called Universal gates because from the use of any of the gate we can easily construct other logic gates.

Realization of logic gates using NAND gate:


i. AND gate.



iii. OR gate.

 


ii. NOT gate.

 


Realization of logic gates using NOR gate:


i. AND gate.

 


ii. OR gate.

 


iii. NOT gate.

 

 Construction of NOR gate using NAND gate.



 Construction of NAND gate using NOR gate.



Q. N. 2.

we have the following truth table of full adder.

X	Y	C _i	S _i	C _{out}
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

We have, $S_i = \bar{X}Y C_i + X\bar{Y} C_i + X Y \bar{C}_i + X Y C_i$
 $= \bar{X}Y C_i + X Y \bar{C}_i + X\bar{Y} C_i + X Y C_i$
 $= \bar{X}Y C_i + X Y \bar{C}_i + X C_i (Y + \bar{Y})$
 $= \bar{X}Y (\bar{C}_i + C_i) + X C_i$

and $C_{out} = \bar{X}\bar{Y} C_i + \bar{X}Y \bar{C}_i + X\bar{Y} \bar{C}_i + X Y C_i$
 $= \bar{X}\bar{Y} C_i + \bar{X}Y \bar{C}_i + \bar{X}Y \bar{C}_i + X Y C_i$
 $= \bar{Y} (\bar{X} C_i + X \bar{C}_i) + Y (\bar{X} \bar{C}_i + X C_i)$

K-Map for S_i

X \ Y C _i	00	01	11	10
0			1	
1		1	1	1


\downarrow $X C_i$ \rightarrow $X Y$
 $\therefore S_i = Y C_i + X C_i + X Y$

K-Map for C_{out}

X \ Y C _i	00	01	11	10
0		1		1
1	1		1	

$C_{out} = \bar{X}\bar{Y} C_i + \bar{X}Y \bar{C}_i + X\bar{Y} \bar{C}_i + X Y C_i$


Implementation using PLA.

 

Q. N. 3.

 
i. $F(A, B, C) = \sum(1, 4, 5, 6)$.

Since the given function has three variables, so we can implement it by using 8:1 MUX.



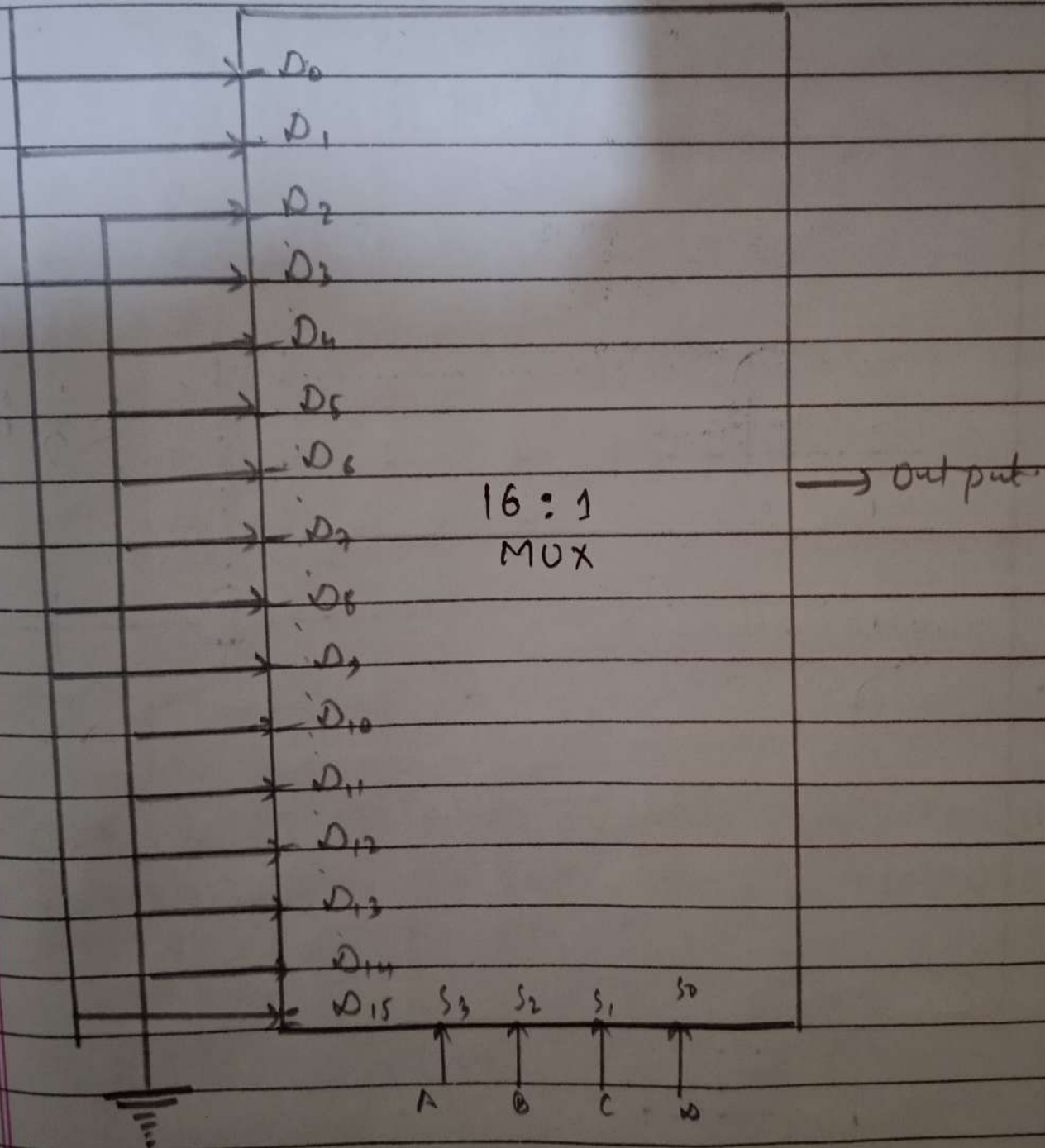ii. $F(A, B, C, D) = \sum(0, 1, 3, 8, 9, 15)$.

Since the given function has four variables, so, we can implement it by using 16:1 MUX + VCC



Q.N.5.

Counter is the sequential ckt that passes through the predefined sequence of state upon the application of input clock pulse.

No. of ^T flip flop required = 4.

$$2^n \geq 10$$

$$2^4 \geq 10$$

Excitation Table of T flip flop

Q_i	Q_{i+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Present state (P.S)				Next state (N.S)				T. inputs			
A	B	C	D	A'	B'	C'	D'	T _A	T _B	T _C	T _D
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1

From above table $T_D = 1$.

K. Map for T_A .

AB \ CD	00	01	11	10
00				
01			1	
11	X	X	X	X
10	X	1	X	X

\downarrow A
 \downarrow BCD

K. Map for T_B

AB \ CD	00	01	11	10
00			1	
01			1	
11				
10				

$\rightarrow \bar{A}CD$

K. Map for T_C

AB \ CD	00	01	11	10
00		1	1	
01		1	1	
11	X	X	X	X
10	X	X	X	X

$\rightarrow \bar{A}D$


$$\therefore T_A = A + BCD$$

$$T_B = \bar{A}CD$$


$$T_C = \bar{A}D$$

$$T_D = 1$$


Q.N.6.

 


(a) Addition.

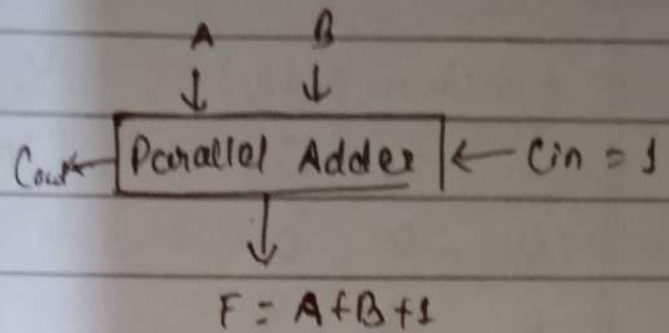


(b) Addition with carry.

 


(c) A plus 1's complement of B.

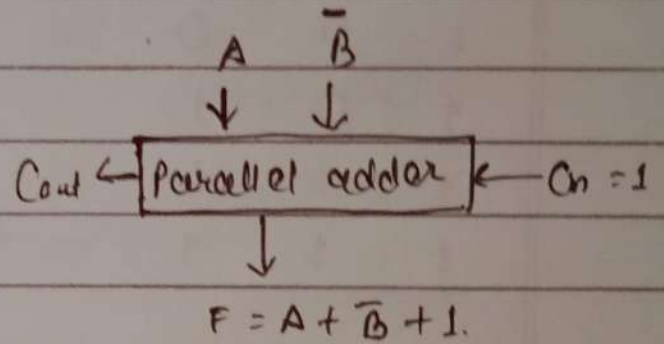


(d) Subtraction.

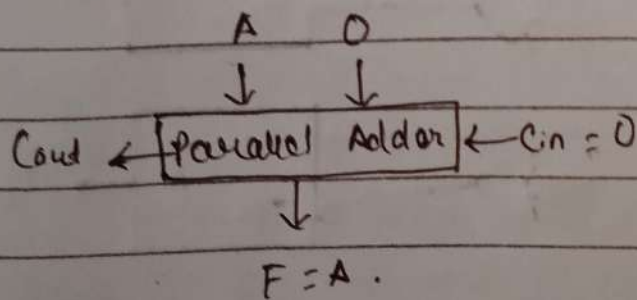


(e) Transfer A.

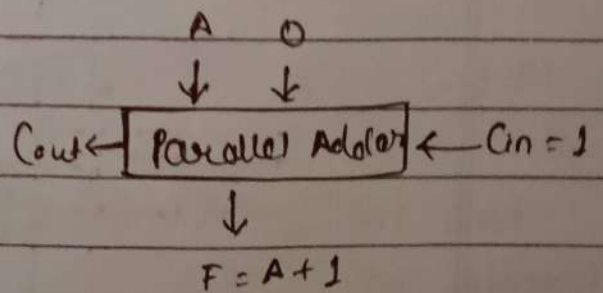

(f) Increment A.

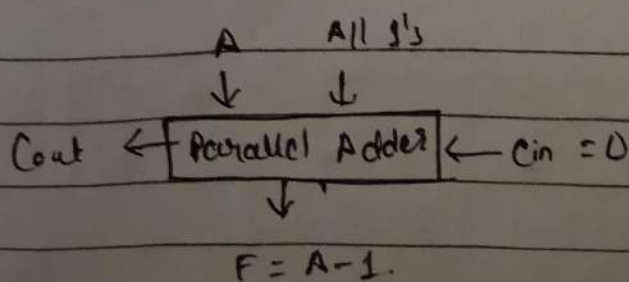


(g) decrement A.

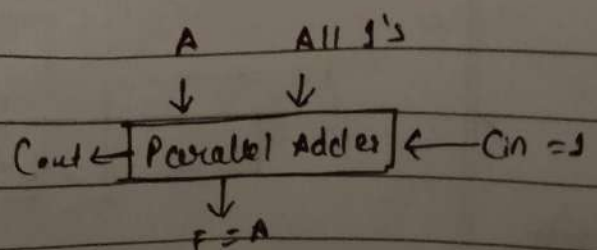

(h) Transfer A.


Function table for arithmetic circuit:

Function select			Y equals	Output equals	Function.
S_1	S_0	C_{in}	(Input)		
0	0	0	0	$F = A$	Transfer A
0	0	1	0	$F = A + 1$	Increment A
0	1	0	B	$F = A + B$	Add B to A
0	1	1	B	$F = A + B + 1$	Add B to A
1	0	0	\overline{B}	$F = A + \overline{B}$	Add 1's complement of B to A
1	0	1	\overline{B}	$F = A + \overline{B} + 1$	Add 1's complement of B to A
1	1	0	All 1's	$F = A - 1$	Decrease A
1	1	1	All 1's	$F = A$	Transfer A

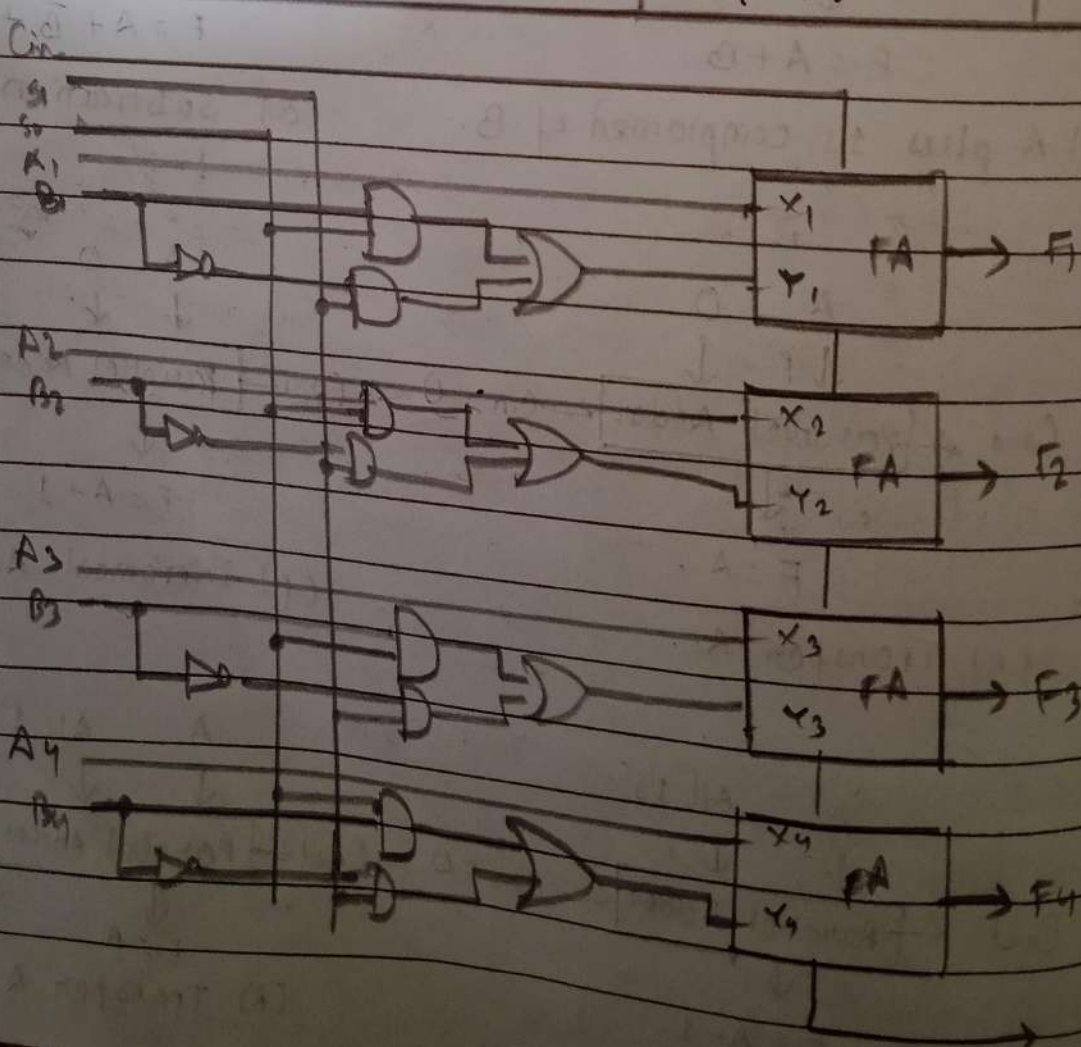

Shift Register:

 A register capable of shifting its binary information either to the right or the left. The logical configuration of shift register consists of a chain of flipflops connected in cascade. A flipflop receives a common clock pulse which causes the shift from one stage to another.



(a) Block diagram of serial transfer of information from register A to register B.

Assume the binary content of A before the shift is 1011 and that of B is 0010. The serial transfer from A to B will occur in 4 steps as shown in table. After the first pulse T1 the rightmost bit of A is shifted into the leftmost bit of B and at the same time, this bit is circulated into the leftmost position of A.

Once the bit of A and B are shift to right, the previous serial output from B is lost.

Timing pulse	Shift Register A	Shift Register B	Serial out
Initial value	1 0 1 1	0 0 1 0	0
After T ₁	1 1 0 1	1 0 0 1	1
After T ₂	1 1 1 0	1 1 0 0	0
After T ₃	0 1 1 1	0 1 1 0	0
After T ₄	1 0 1 1	1 0 1 1	1